



K. K. Wagh Polytechnic, Nashik

Hirabai Haridas Vidyanagari, Amrutdham, Panchavati, Nashik-422003

Department of Artificial Intelligence & Machine Learning

Date: 16/11/2024

Academic Year: 2024-25

Course & Code: Digital Techniques (DTE -313303)

Semester & Code: AN-3-K

Class: SYAN

Sem: III(ODD)

Question Bank for Practical End Semester Examination Winter-2024

1. Test the functionality of specified logic gates using breadboard.
(IC 7404, 7408, 7432)
 - a) Write down voltage at logic level 0 & 1.
 - b) Draw the symbol & Truth Table of NAND & NOR Gate.
2. Test the functionality of NAND & NOR logic gates using Breadboard.
(IC 7400, 7402)
 - a) Design 3 input NAND gate using 2 input NAND Gate.
 - b) Draw Symbol & Truth Table of AND, OR & NOT Gate
3. Construct AND, NOT gates using NAND gates.
 - a) Draw IC pin diagram of NAND gate(IC 7400)
 - b) State Demorgan's theorems.
4. Construct OR, NOT gates using NOR gates.
 - a) Draw IC pin diagram of NOR gate(IC 7402)
 - b) Write Truth table & Symbol of AND & NAND Gate
5. Verify De-Morgan's First & Second theorem.
 - a) List the IC numbers used in Demorgan's First & Second theorem
 - b) Write Truth table & Symbol of AND, OR & NOT Gate.
6. Design Full Adder using Boolean expression.
 - a) Draw full adder & its truth table.
 - b) Design half adder using K-map
7. Design Half Subtractor using Boolean expression.
 - a) Draw full subtractor & its Truth table.
 - b) Design half subtractor using K-map
8. Build/ test functionality of MUX74151
 - a) List the function of Pin 5,6 & 7 of IC74151
 - b) What is DEMUX?
9. Build/ test functionality of DEMUX74155/74154
 - a) List the function of Pin 2,3 & 5 of IC74154
 - b)What is MUX?
10. Build/ test functionality of RS Flip-Flop.
 - a) What is drawback of RS Flip Flop?
 - b) Draw the circuit diagram & Truth Table of JK Flip Flop

11. Use IC 7476 to construct and test functionality of D Flip-Flop & T Flip-Flop.
 - a) What is Race around Condition?
 - b) Draw the circuit diagram & Truth Table of SR Flip Flop.
12. Implement Ripple counter using Digital IC
 - a) Draw timing diagram for 4 bit up ripple counter.
 - b) give the applications of counter
13. Implement Decade counter using Digital IC
 - a) Draw timing diagram for decade counter
 - b) What is mod 5 counter, write it's truth table.

M.N.Jadhav
Subject Teacher